

17007(M)

B. Tech 2nd Semester Examination

Fundamental of Electronics Engineering (CBS)

EC-101

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt five questions in all, selecting one question each from section A, B, C & D. Section E is compulsory.

SECTION - A

1. (a) What do you mean by intrinsic and extrinsic semiconductor? What is the effect of temperature on semiconductor? (6)
- (b) What are the two types of capacitance across a P-N junction? Explain in detail. Which of these is more important in case of forward bias? (6)
2. (a) Define Filter. Explain LC and π filter in detail. (6)
- (b) What do you understand by LED? Draw its symbol. Explain principle, working and characteristics of LED. Write its applications also. (6)

SECTION - B

3. (a) What is current amplification factor? Derive the relation between Beta and Alpha of a transistor. (6)
- (b) What do you mean by depletion and enhancement MOSFET? Explain their construction, working and characteristics. (6)

2

17007

4. (a) A germanium transistor used as an amplifier has a collector cut off current $I_{CBO} = 10\mu A$ at a temperature $27^\circ C$ and $\beta = 50$.
 - (i) What is the collector current when the base current is $0.25mA$?
 - (ii) Assuming that β does not change with temperature, what would be the value of new collector current, if the transistor's temperature rises up to $50^\circ C$? (6)
- (b) Draw and explain Static characteristics and transfer characteristics of N-channel JFET. (6)

SECTION - C

5. (a) Draw the circuit diagram of Wein bridge oscillator using transistor and explain its operation by deriving expression for frequency of oscillation. (6)
- (b) Draw the equivalent circuit of an OP-AMP and explain the various parameters used in the equivalent circuit. (6)
6. (a) What do you understand by closed loop and open loop gain of an OP-AMP, when a Non-inverting OP-AMP acts as a voltage follower? <https://www.hptuonline.com> (6)
- (b) Draw and explain the circuit of a tuned plate oscillator. Explain how oscillations originate in this circuit. (6)

SECTION - D

7. (a) State and prove the De-Morgan's theorem. (6)
- (b) Draw and explain the block diagram of Cathode Ray Tube & Write its uses. (6)

8. (a) How do you measure unknown phase and unknown frequency using CRO? Explain properly. (6)
- (b) What is Half adder? How is it realized using logic gates? Design a full adder circuit using NAND gate. (6)

SECTION - E

9. (a) Explain the frequency stability in Oscillators.
- (b) Which gates are known as universal gates and why?
- (c) Define static and dynamic resistance of Diode.
- (d) Differentiate CB, CC, and CE configuration.
- (e) Comparison of P-channel and N-channel MOSFETS.
- (f) Describe the ideal characteristics of an OP-AMP. (2×6=12)