

**D-C-190009****B. Tech. EXAMINATION, 2019**

Semester I &amp; II (CBS)

**PRINCIPLES OF ELECTRICAL ENGINEERING**

EE-101

Time : 3 Hours

Maximum Marks : 60

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

**Note :** Attempt Five questions in all, selecting one question from each Section A, B, C and D. Q. No. 9 is compulsory.

**Section A**

1. A d.c. source has an open-circuit voltage of 30 V and an internal resistance of 1.5. State the value of load resistance that gives maximum power dissipation and determine the value of this power. **10**

2. How Voltage and Current Sources represented ? What is the difference between an ideal and practical voltage source ? **10**

**Section B**

3. Draw Phasor diagram and voltage triangle for an LR series circuit. Derive an expression for Instantaneous and Average power in a series LR circuit. **10**
4. What are the advantages of 3-phase system ? Compare Star and Delta Connections. **10**

**Section C**

5. State Ampere's Law. How do you use the law to define a flux line and flux density ? **10**
6. How do you calculate the power factor of the balanced load from wattmeter readings ? **10**

**Section D**

7. A transformer takes a current of 0.8 A when its primary is connected to a 240 volt, 50 Hz supply, the secondary being on open circuit. If the power absorbed is 72 watts, determine :
  - (a) The iron loss current
  - (b) The power factor on no-load
  - (c) The magnetizing current. **10**

8. Derive expression for generated e.m.f. in armature winding of a DC machine.

10

### Section E

#### (Compulsory Question)

9. (a) Distinguish between Apparent and Active Power.  
(b) State *two* advantages and *two* disadvantages of moving coil instruments.  
(c) Define Q Factor of a series resonant circuit.  
(d) What are the implications of Thevenin's Theorem ?  
(e) Define Relative Permeability.  
(f) List *three* types of damping employed in electrical instruments.  
(g) State Torque equation of an Induction Motor.  
(h) Define Node, Path, Branch and Mesh for Electrical Circuit.  $2\frac{1}{2} \times 8 = 20$  ( $2\frac{1}{2}$  marks each)

<https://www.hptuonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से